

A VHF/HF Aerial Analyser

Jim Tregellas VK5JST

At long last, the 1948 show! No, seriously, I have had a lot of fun developing this analyser which covers all amateur bands from 160 to 2 metres, and won't entirely break the bank.

It features a 1602 LCD display which, like the previous HF analyser, is updated every 100 milliseconds, and shows frequency, SWR, load resistance, and the magnitude of the load reactance. An optional analogue meter is also provided,


which shows the magnitude of the load impedance (Z total).

This data has many uses, and as an example, allows impedance minimums to be very accurately located. So it will display the antenna load resistance, when the total load impedance of an antenna system has been minimized by careful tuning and also allows easy development of items like quarter and half wave stubs and measurements like velocity factor.

In combination with the analyser frequency data, it is a very powerful tool.

Readily available through-hole components are mainly used in the construction, and just five surface mount components have to be fitted. And like the previous analyser, a PICAXE processor is used, which is loaded with dear old BASIC through a very simple two resistor interface, allowing anyone to play with the code without having

Photo 1: Inside the Analyser.

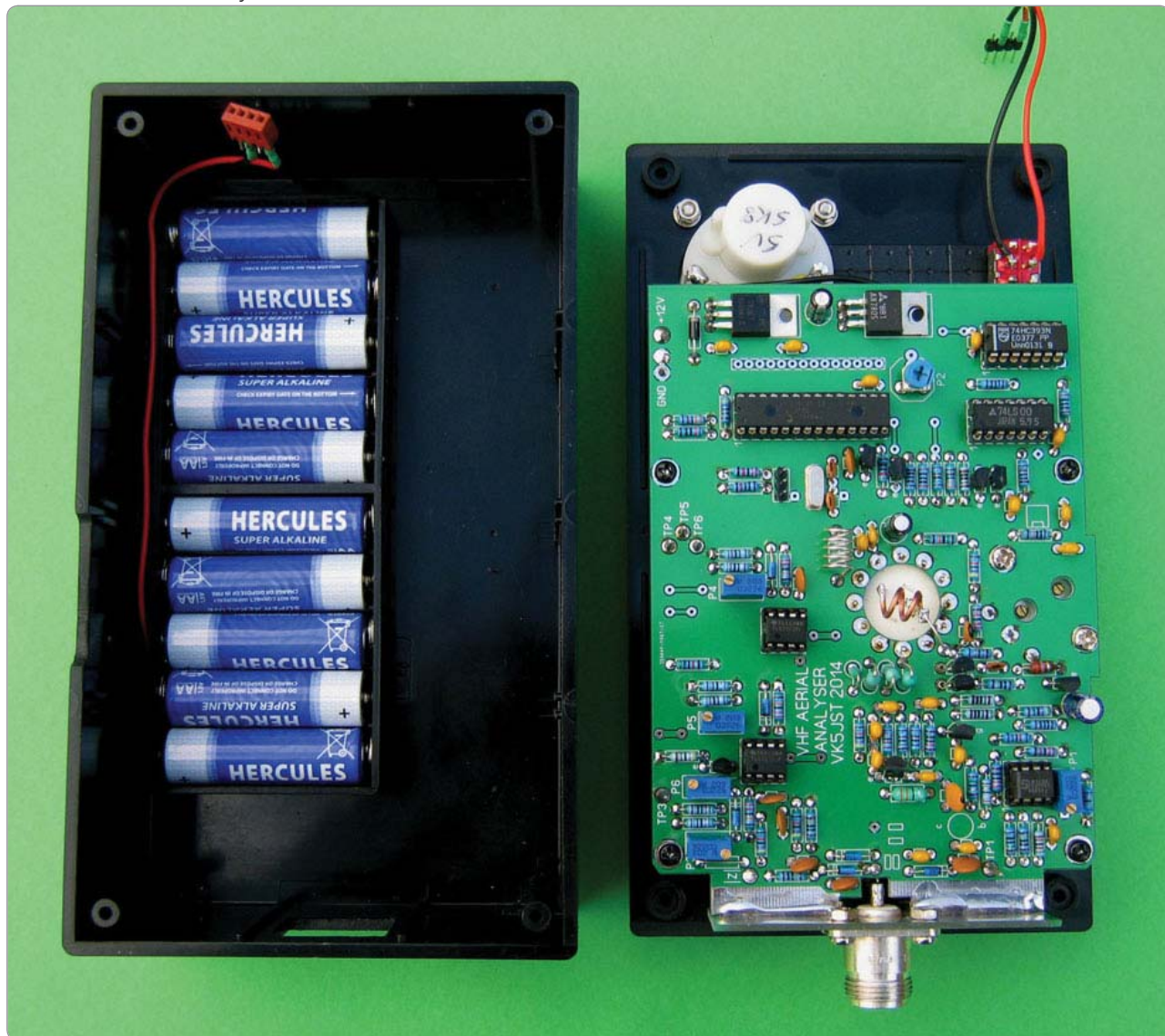

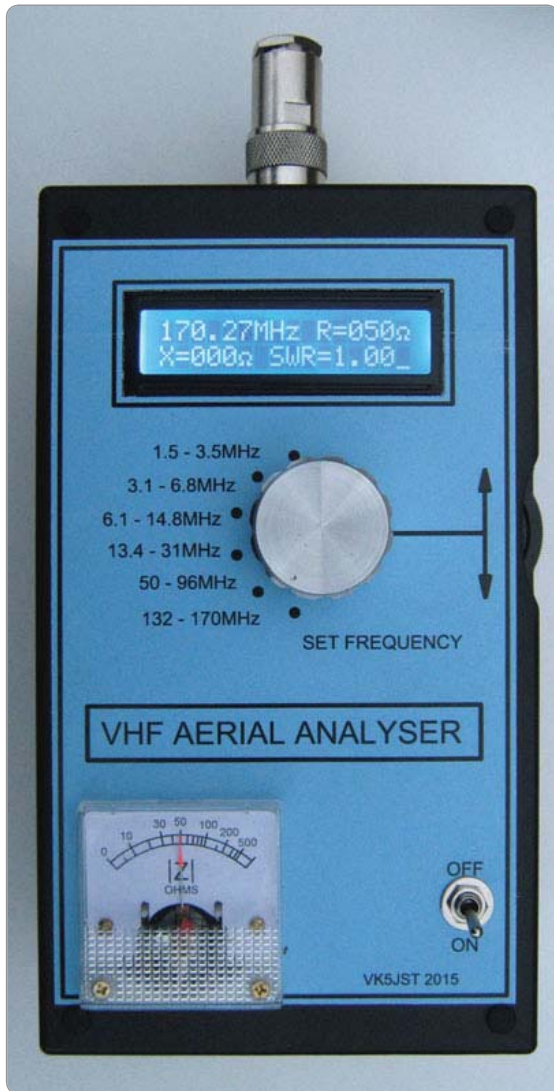


Photo 2: The front of the Analyser.

to buy special programming tools, or learn an abstruse language like C or assembler.

Finally, the analyser uses the best 50 ohm connector around, the type N which is both waterproof and constant impedance. Adapters can be purchased for other VHF quality connectors (BNC, SMA etc.) but please don't fit it with a type SO239. This so-called UHF connector (40 MHz at the time of design) is not constant impedance and simply does not belong on VHF test gear.

The basic theory

As in the previous analyser, the SWR, load resistance, and magnitude of the load reactance are derived mathematically by measuring three voltages in a simple test circuit. First, the voltage across the load is measured, as is the voltage across a 50 ohm series resistor (from which load current can be derived).

Finally the voltage existing across both the load and 50 ohm series resistor is measured (test network input voltage). The moderately complex mathematics

ONE-STOP-SHOP

Bargain Packs

A great collection of spare components and odds & ends. Replenish your own collection with our handy bargain packs.

Switches Pack (50 pc)

XB-9007 \$14.95

MKT Capacitor Pack (90 pc)

XB-9008 \$19.95

Heatshrink Pack (15 pc)

XB-9009 \$9.95

FROM \$9.95
NEW

XB-9009



LED Magnifying Lamp with Third Hand

Just like having a third hand while soldering.

Features alligator clips to hold the project, LED illuminated 90mm 3x magnifying glass, soldering stand and more.

Visit our website for more details

- 4 AA Batteries required (SB-2357 \$19.95)

XB-9006

\$39.95
NEW



Battery Organiser with Tester

Store your batteries easily with this organiser. It can be hung on a wall or placed flat in a drawer. It includes a removable tester.

- Holds 8xD, 10xC, 25xAA, 10xAAA and 8 x 9V batteries

QP-2312

\$14.95
NEW



*Batteries not included

LED Voltmeter and Ammeter

Monitor your battery voltage and current draw easily. Simply follow the wiring diagram to measure 5-30VDC, and 0 to 10A DC. Built in shunt.

- Panel/surface mount hood supplied

QP-5584

\$39.95
NEW



LED Headband Magnifier

This magnifying headset leaves both hands free and can be worn over prescription or safety glasses.

- Adjustable head strap
- Built-in LED work light
- 1.5x, 3x, 8.5x or 10x magnification
- Requires 2 x AAA batteries (SB-2355 \$11.95)

QM-3511

\$29.95



13.8VDC Regulated Power Supplies

High powered 13.8V switchmode power supplies delivering up to 40A. Suitable for development and test environments.

Internal cooling at higher outputs.

12A MP-3079 \$69.95

20A MP-3078 \$99.95

40A MP-3089 \$199



MP-3079

FROM \$69.95

Prices valid until 30th November 2015
 To order call 1800 022 888 or visit
www.jaycar.com.au

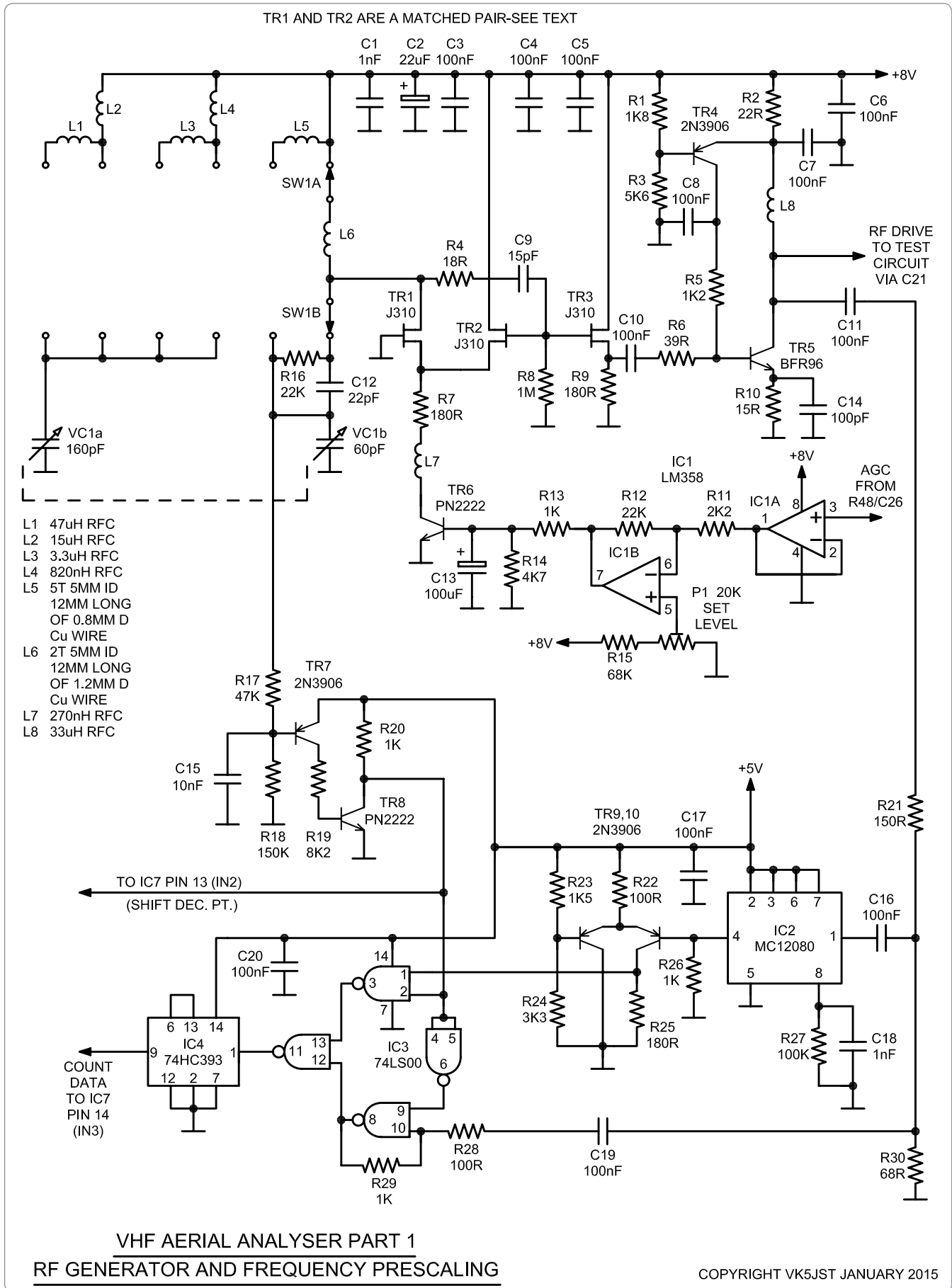


Figure 1: The circuit diagram of the RF generator and frequency prescaling.

for deriving SWR and load R and Z from these three voltages is up on my website, and in the previous HF analyser article, and will not be repeated here.

And, unlike the beliefs of some Internet "experts", only a series resistor is required to do this, and NOT a Wheatstone bridge. The balanced structure of this bridge adds nothing to the accuracy of these measurements.

Note that the voltage measured across the load also provides a non-linear representation of total load impedance and can be used to directly drive the analogue meter too.

How it works

This test network is the heart of the instrument structure, and a very wide range frequency generator provides 1 volt RMS to drive it. This signal level has been selected to totally bury all but the most exceptional interfering signals on

the antenna being tested, without flattening the batteries too fast.

Unhappily, analogue meters display the absolute value of applied voltage, and so the generator and following test circuit detectors must have a stunningly good frequency response, remaining flat within 1% or so over the total frequency range, so that the analogue meter display of magnitude of load impedance is correct. The oscillator and following power amplifier consequently must have a first class AGC system.

(In a digital only instrument all calculations use the RATIOS of the various test circuit voltages and so this requirement is relaxed greatly allowing a simpler cheaper but less useful instrument).

The oscillator uses a differential amplifier containing a matched pair of VHF FETs (TR1 and TR2). A parallel tuned circuit in the source of TR1 maximises the gain of this transistor pair at a single frequency and the positive feedback path

to create oscillation occurs via the source follower action of TR2 which couples energy back to TR1 via the coupled sources of these two transistors. Another source follower, TR3, buffers the oscillator output from the tuned circuit and drives the power amplifier TR5. This amplifier has a special and unusual bias circuit TR4, which samples the current drawn by TR5 via R2 and sets the collector current of TR5 to the 57 mA required to drive the 50 ohm test circuit with 1 volt RMS, providing some design margin and very little waste. Note that this amplifier has a permanent load composed of 2@100 ohm resistors which are there to limit the amplifier voltage gain when the test circuit has no load. The generator must thus provide 1 volt RMS (with margin) into 40 ohms (+14 dbm) when the item being tested is a short circuit.

AGC to control this structure is developed from a DC voltage



www.ttssystems.com.au

Phone: 03 5977 4808 Email: info@ttssystems.com.au

Your Australian reseller for:



BUDDIPOLE



Mean Well power supplies
Diamond products
Daiwa products
Technical books
Amidon products
Custom cables made to order



Merry Christmas & a Happy New Year 2016

Visit our **new website** at www.ttssystems.com.au

YouKits
NEW PRODUCTS

AVAILABLE NOW

Hard Drawn Copper Wire, Insulators,
Open Wire Transmission Line, Spreaders, Kevlar Guy Line,
Spiderbeam Fibreglass Poles, Baluns and Switches


produced from envelope detector D1, C23, and R47. This DC voltage represents the peak value of the RF voltage being applied to the test circuit and is buffered by unity gain amplifier IC1A. The output voltage of this stage is compared with a DC control voltage appearing on pin 5 of the inverting amplifier IC1B (gain of 10). In turn the output voltage of this stage is applied to the base of TR6, which determines the total current flowing through TR1 and TR2, hence determining the total gain of the differential pair and the level of oscillation. The level of oscillation is adjusted with trim pot P1.

The entire detector outputs from the test circuit (derived from D1, D2, and D3) provide DC outputs which are in turn buffered and have their considerable non linearity's largely compensated for in some following op. amp. circuitry (IC5 and IC6). These three compensated DC output voltages then drive the analogue meter, and the A/D converter inputs of the microprocessor, from which SWR and load characteristics are calculated.

Finally, the generator frequency is calculated every 100 milliseconds or so by the microprocessor. For

frequencies under 30 MHz, a voltage sample from the input to the test circuit is directly routed to IC4 (74HC393) via an amplifying and steering circuit IC3 (74LS00) where it is divided by 256 before being fed to the microprocessor for counting and gating. For frequencies above 30 MHz, some extra high speed pre-scaling is required, and this is done using an ECL decade divider chip IC2 (MC12080). This chip is followed by a non-saturating ECL to TTL translator stage (TR9 and TR10) which in turn provides the second input to the IC3 steering stage. The pre-scaler structure in use is

Figure 2: The circuit diagram of the test circuit, detectors and metering.

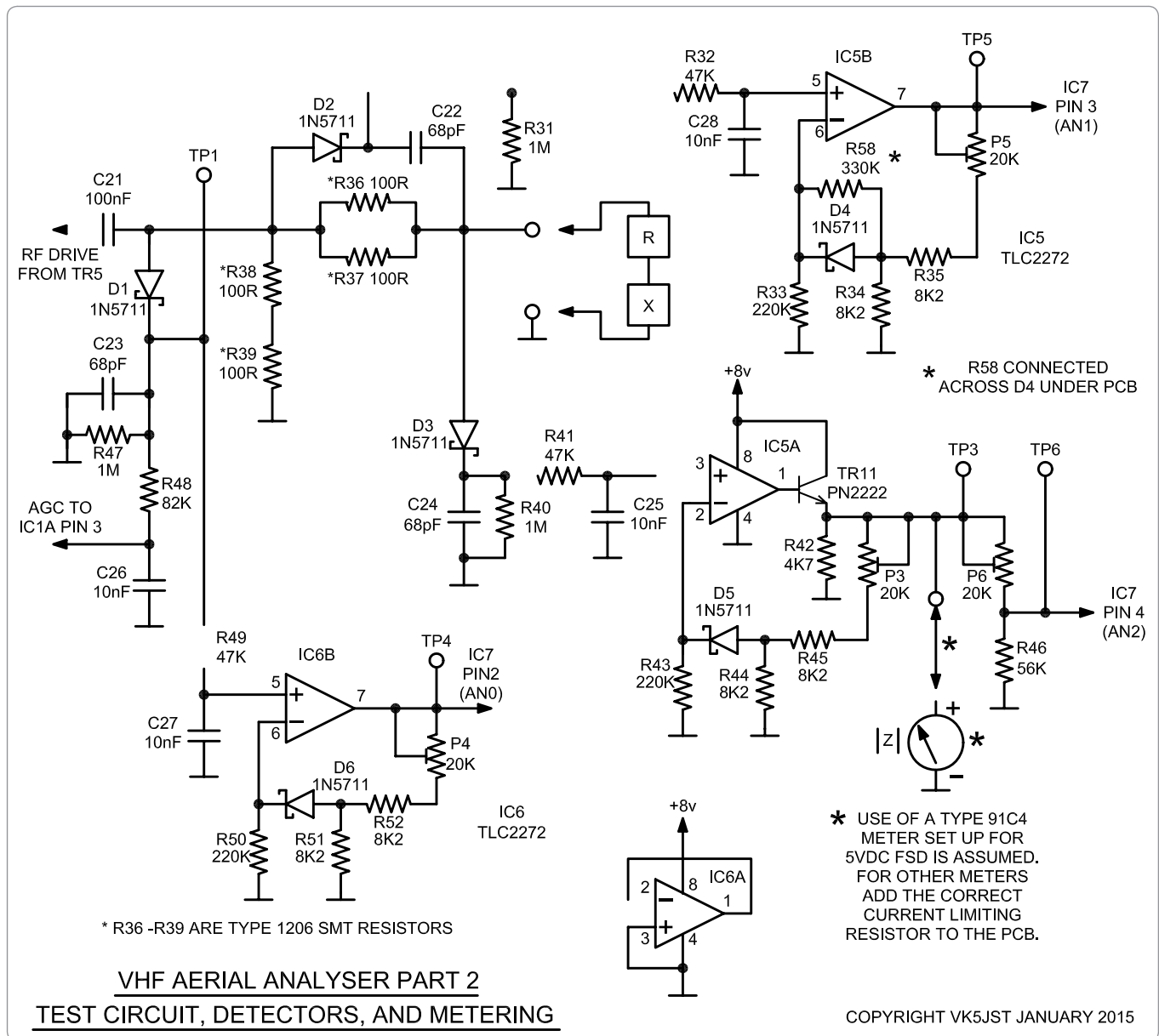

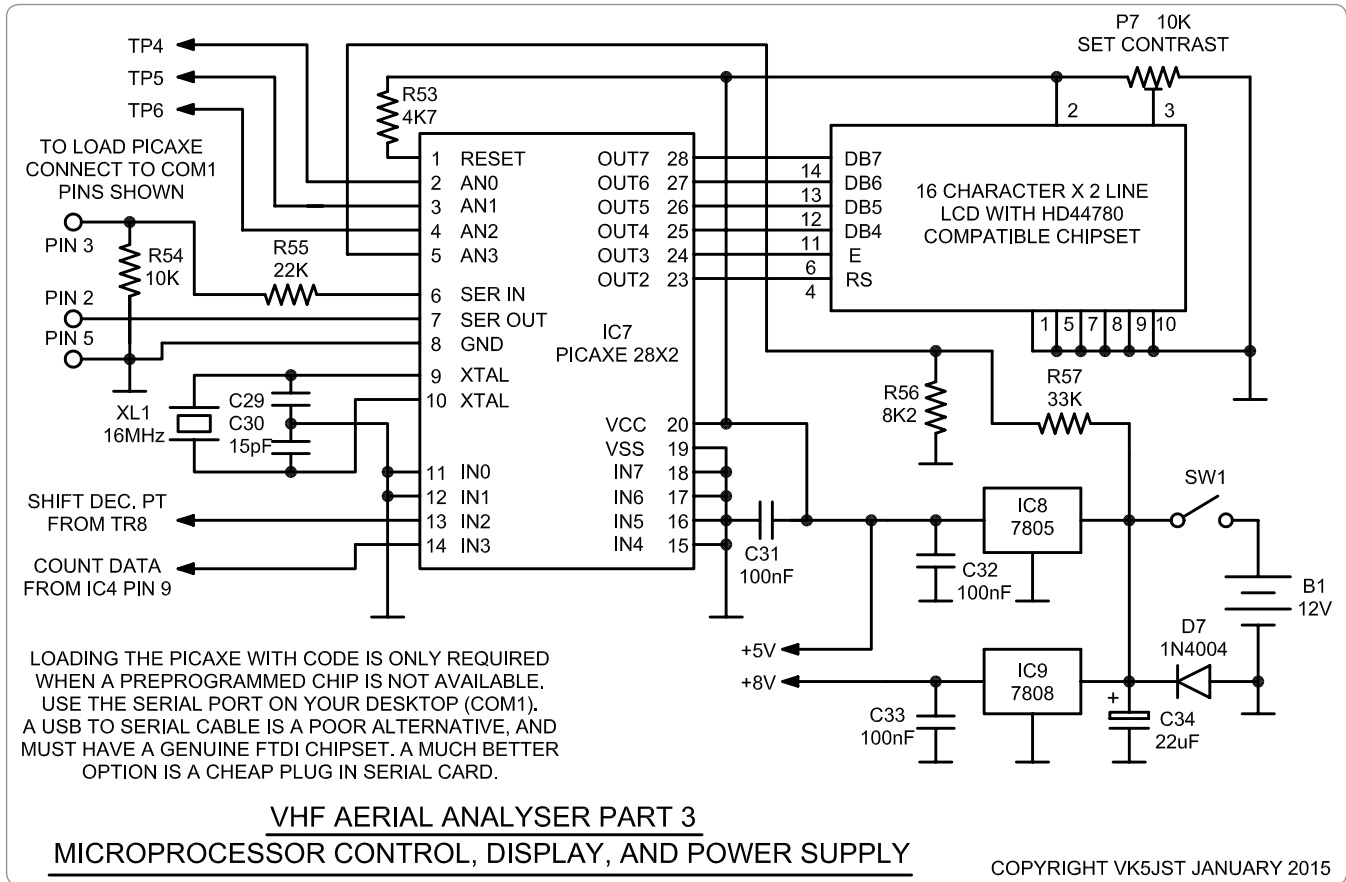


Figure 3: The circuit diagram of the microprocessor control, display and power supply.

TET-EMTRON

Kits!
Kits!
Kits!

New Hanging Dipole Kits!!!



Make your own dipole centre using the new kit. All the parts are there including insulators in some kits. Just bring your own wire.

- Gold pin connector
- Glue lined heatshrink.
- Tinned solder tabs.
- Stainless hardware.

Perfect for club project days.

- All the standard high quality TET parts you expect including stainless hardware.
- Full instructions.
- A range of ferrites
- Parts also available separately.
- Club discounts apply

TET-Emtron
47 Ocean Drive,
PORT DENISON.
W.A 6525
08 9927 1872
See our wide range of new parts and products at:-
www.tetemtron.com.au

Balun Kits!



More and more Kits coming every month!!!

determined by a logic level derived from the tank circuit of the oscillator. For the two upper frequency ranges, the 8 volt supply rail is connected to the base of TR7 via resistors. TR7 is thus off, as is TR8, and so pins 2, 4, and 5 of IC3 are pulled high via R20, connecting the output of IC2 to the input of IC4 via IC3 and adding the extra pre-scaling. Note that the logic level at TR8 collector is also supplied to the microprocessor to shift the decimal point in the displayed frequency.

Building the Analyser-mechanical work

Complete all work on the case first.

Doing assembly in this order allows you to use the bare printed circuit board to check marking out. Marking out is probably most easily done by printing up the case drawings exact size, and attaching them to the correct surfaces of the UB2 box with thin double sided tape. A very sharp scribe can then be used to prick through the hole centres or corners into the plastic. Check the exact size of the LCD you have decided to use. The front panel drawing shows the 24 x 71 mm hole used by industry standard LCDs but yours may be different. For all circular holes, drill a small pilot hole first (around 1.5 mm dia.) using the pricking to centre the drill, and then slowly open out to final size using either a larger drill, or for larger holes, a step drill, fly cutter or hole saw. Using ordinary metal working drills in this sort of plastic is dangerous. Clamp all work and use slow gentle feed rates while drilling.

Use a grinder to reduce the rake angle on the drill leading edges to zero, which will stop the drill grabbing and trying to rip the box out of the holding clamps. The holes for the LCD and N connector can be roughly formed with a jig saw first or by drilling a series of nearly touching holes (around 5-6 mm dia.) just inside the borders of the rectangular hole. It is then carefully filed to final shape. The cut-out for

the tuning knob in the case lid is probably best formed with a half round file. Find something around 80 mm diameter (a tin can or cup) and use this to keep an eye on the circular shape as you file this arc to a depth of 4 mm. The arc can be smoothed off with fine sandpaper to finish it. The case bottom has two items to be formed, the cut-out for the tuning knob in the top surface of the right hand side, and the hole for the type N or BNC connector in the top end of the case.

Please see the relevant drawings.

Building the Analyser - initial preparations

The Rotary Switch

In past designs, the plastic rotary switch used for frequency range selection has caused much confusion because builders will not take the time to learn how to set them up properly. The 6 position 2 pole switch used in this instrument can be rotated through twelve possible positions, and so rotation can either start clockwise from position 1 or anti clockwise from position 12.

Just how many positions are available is determined by an adjustable travel limiting stop to be found under the main mounting nut. So you can make any 2 pole switch with from 2 to 6 positions, starting either at pin 1 or pin 12. To set up the switch in this instrument, first remove the adjustable stop entirely and then, looking at the front of the switch, rotate it fully clockwise to position 12. Then put the travel limiting stop into position 6 (between the L and P in the ALPHA brand). Done!

Note how it is placed into the printed circuit board with the central common terminals being placed at the 4 and 10 o'clock positions, looking at the back of the switch on the component overlay drawing, with the N connector at the top of the diagram.

BEFORE you solder it into

position, check with your ohm meter that the common terminal at 4 o'clock bridges to the 6 outer terminals between 12 and 5 o'clock. The common terminal at 10 o'clock will thus sweep through the switch positions from 6 to 11 o'clock.

Make a mistake here and you may very well wreck the PCB when you try to de-solder the switch from it. And finally make your soldering quickly. These switches go open circuit when exposed to excess soldering temperature/times.

The optional analogue meter

The meter used is available very cheaply on the "net" and typically can be bought as a type 91C4 or 91L4 with a built in series resistor for 5 volt FSD. This meter just requires rescaling and here is how. Buy a single A4 Avery label sheet (80- 100 gsm) from your local stationer, and print the meter scale on to it from the PDF to be found on my website.

With a very sharp pointed hobby knife cut out the meter scale.

In a CLEAN environment, remove the meter face and scale. Remove the label backing, exposing the sticky back. The label goes on the back of the existing scale. Carefully align the top of the label with the top of the meter scale and then stick the two together, removing all air bubbles. Cut around the bottom of the assembly with the point of a very sharp hobby knife and then reassemble the meter.

If you cannot get a 91C4 meter with a 5 volt scale, note that any 91C4 meter with a voltage scale can be used. All you have to do is remove the internal series resistor (see the photo on my website) to convert the volt meter back to a current meter.

The correct resistor to give full scale deflection with 5 volts DC applied is then added to the PCB in the position marked "TEXT". Depending on exactly which meter you bought, this resistor could be anywhere from 2-100 kΩ. Start at the high value first. For 5 V FSD

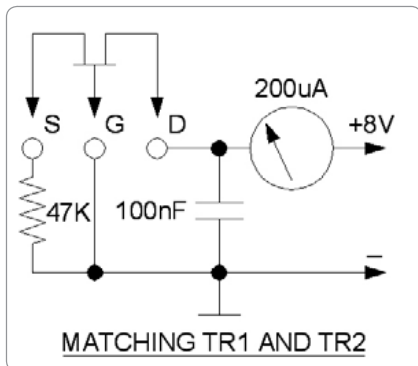


Figure 4: The circuit for matching the current characteristics of the FETs TR1 and TR2.

meters, the PCB “TEXT” positioned is bridged with a shorting link.

Matching TR1 and TR2

It is vitally important that these FETs are carefully matched. Failure to do so will result in an oscillator/power amplifier which probably works correctly on the upper two frequency ranges but “squeggs” on all other ranges i.e. puts out short bursts of RF at a low audio frequency. This occurs because the AGC is unable to back off the oscillator gain enough, owing to the mismatched devices.

DO NOT mix brands when matching.

I bought a batch of 20 J310 FETs from the “net” and matched them up using the simple circuit shown in a standard prototyping whiteboard. The spread in current was from 50-92 micro amps over the batch. I matched up three pairs at 53, 73, and 94 micro amps within 1.0 microamp and experienced no problems with squegging in the analyser. I used the 73 micro amp pair in the final prototype. Note the bypass capacitor in the test jig. Without it the FET may oscillate at VHF, upsetting the matching. Make sure it is connected directly between gate and drain with the shortest leads possible.

The coils

The coils for the two upper frequency ranges are wound on the shank of a 5 mm drill. The highest

range uses a 44 mm length of 1.2 mm dia. copper wire formed into two turns and quickly soldered between the two common terminals of the rotary switch.

Do this BEFORE mounting the switch on the main PCB. The other coil comprises 5 turns of 0.8 - 1.0 mm dia. copper wire. Carefully scrape and tin the ends of both coils before assembly.

Final Assembly

First, solder the connector printed circuit board to the mainboard. Use the two alignment ears provided at the edges of the connector board copper pattern to exactly centralise it relative to the main board, and tack it into position using minimum solder. Check that the two boards are at right angles and then complete all soldering forming four strong bonds between the two boards. Use at least a 45 watt iron for this.

Next, add all small components to the PCB using the component overlay and circuit drawings as guides.

ASSUME NOTHING!!!

Use your DVM to check the value of every resistor before installation.

Depending on who made them, the PN2222 and 2N3906 come with two different pinouts and for this reason, the locating flats on these transistors are not shown on the component overlay. Check the pinout of your transistors using the current gain feature on your DVM. An indicated current gain of more than say 40 shows you have the correct pinout. The BFR96 is mounted on the track side of the PCB with its label facing the PCB surface. Trim the three leads to an appropriate length. The collector is the long lead.

USE IC SOCKETS. Note that the MC12080 and 4@100 ohm surface mount resistors are also mounted on the track side of the PCB. The lead lengths of all capacitors should be kept as near to zero as possible. Do not expect the analyser to work

HAM RADIO HOUSE

The Boatanchor shop!

www.hamradiohouse.com.au

Email: hamradiohouse@tpg.com.au

Phone: Stephen, VK2LSC on 0414 392653

PO Box 1357, PENRITH NSW 2751

Receiving Valves (NOS except as noted)

OB2	\$9.00	6AQ5A	\$10.00
OA2	\$9.00	6AN8	\$10.00
8BN8	\$8.00	6AF4	\$9.00
7360	\$34.00	5Y3GT	\$20.00
6U8 (A)	\$8.50	5AR4	\$28.00
6SK7	\$8.00	13DE7	\$8.00
6SH7	\$8.00	12DK6	\$8.00
6SG7	\$8.00	12BZ6	\$18.00
6SC7	\$17.00	12BY7	\$20.00
6SA7	\$12.00	12BE6	\$12.00
6K6GT	\$9.00	12BA6	\$12.00
6JH8	\$9.00	12AX7	\$25.00
6H6GT	\$9.00	12AU7	\$25.00
6GK6	\$14.00	12AT7	\$20.00
6EW6	\$8.00		
6EV7	\$8.00		
6DC6	\$12.00		
6D10	\$19.00		
6CX8	\$8.00		
6CA4	\$25.00		
6BZ6	\$10.00		
6BV8	\$12.00		
6BN8	\$15.00		
6BE6	\$7.50		
6AW8	\$7.50		
6AU6A	\$9.00		

Transmitting Valves

6146B US	\$55.00
6146B CH	\$35.00
2E26	\$12.00
G-807	\$16.00
6JEC6	\$65.00

Ceramic Octal, 7 pin and 9 pin sockets from \$2.75

MSP/OAK NOS

vibrators 4,6 pin

6/12v limited range



\$25.00+P&P



DRAKE

R4B/GENERAL

Replacement Transformer 190-0-190 v 3 filament windings

\$88.00 + P&P



AIRCORE
INDUCTOR 40uH

\$25+P&P

Much more on the site (and off) so call!



ZL1CVD DDS VFO

(assembled)
\$78.00 + P&P

properly if you have used anything other than the multi-plate monolithic bypass and coupling capacitors specified and/or have the capacitors sitting up in the air on the end of 4 mm long leads.

Mount all of the trim pots with their adjustment screws in the position shown on the component overlay. This will allow you to reduce each test voltage by rotating the screws in an anti-clockwise direction.

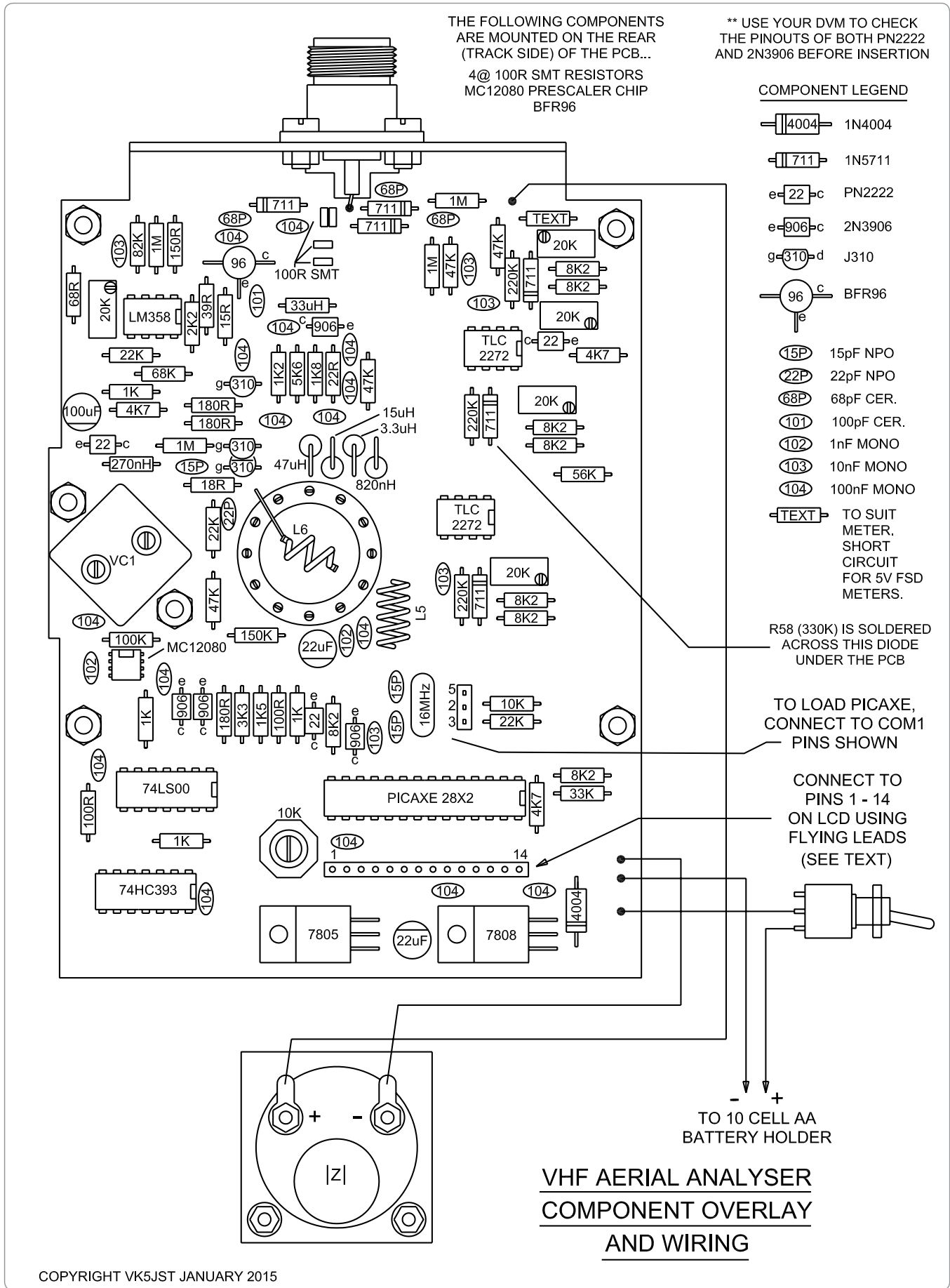


Figure 5: Component overlay and wiring diagram.

When adjusting a 25 turn trim pot, it is very easy to become totally confused if you do not take this simple precaution.

Do not plug in any ICs yet. Double check the orientation of all diodes and electrolytic capacitors. Leave the mounting of the tuning capacitor and rotary switch until last. Before you mount the tuning capacitor on its little daughter board, adjust the two trimmer capacitors at the back of the capacitor so that they are totally out of mesh. Attach the tuning capacitor assembly to the TRACK side of the main PCB using 12 mm long spacers. Last, mount the rotary switch assembly (switch and 2 turn coil) on the TRACK side of the pcb making sure that the two common terminals are positioned as shown on the component overlay at 4 and 10 o'clock (see also the earlier paragraph "The Rotary Switch").

Attach the N connector to its PCB with 3 mm screws and nuts, and connect the central terminal to the main board using the shortest length of wire possible.

Finally solder on all main board flying leads, using 180 mm lengths of multi-coloured hook up wire.

Assemble the front panel. Mount the meter and on/off switch.

Mount the LCD to the front panel using two thicknesses of 2 mm thick double sided foam tape at the display top and bottom (from your local "Cheap" shop). Add the four 30 mm long screws which support the main board to the front panel using 4@ 3 mm nuts. Use another 8 nuts to space and hold the main board away from the front panel by 21 mm.

Complete all wiring. Note that it is possible to interconnect the LCD and main board using 9 wires instead of 14, provided that you connect all of the earthed points together on the display. As both +5 V and ground are available at the display terminals, it is also a simple matter to add backlighting if your display has it.

To do this, ground pin 16 (if your display has a standard pin out). Assuming that the LCD has around 100 ohms of LED current limiting resistance built on to its PCB, battery life can be maximized by placing another 120 ohms between +5 V (pin 2) and pin 15.

Finally attach the 10 cell battery holder to the bottom of the box, again using 2 mm thick double sided foam tape.

Testing and Setup

Select the lowest frequency range and insert IC1 only. Monitor the total current drawn with a DVM (2 amp range). Switch on. The total current should be under 100 mA if all is well and the upper line of the LCD should show a row of black squares after the contrast trim pot has been set correctly. Check TP1 with a DVM and adjust P1 until 1.17 volts appears there. Check the output with an oscilloscope for 2.8 volts peak to peak (1 volt RMS) of good clean sine wave that should now be present. Switch through all frequency ranges and then

smaller - lighter - universal

High Quality Made in Germany

Multiband 13cm Transverter

Just in time for Christmas our new Transverter module for 2.3 GHz EME!

NEW

Merry Christmas and a Happy New Year 2015 from the hole Team!

shop.kuhne-electronic.de

Kuhne electronic GmbH
Scheibenacker 3 Telefon: +49 (0) 9293 / 800640
95180 Berg - Germany E-Mail: info@kuhne-electronic.de

KUHNE electronic
MICROWAVE COMPONENTS

Solutions for the wireless world

go back to the lowest frequency range. The voltage at TP1 should remain within 1% (1.16- 1.18 volts) indicating a very flat RF output level over the total frequency range.

Switch off and add all other ICs except the PICAXE processor.

Switch on.

Set TP4 to 4.40 V using P4. Then using P3 set TP3 to 5.00 V (no meters) or full scale on the "Z" meter. The voltage at TP3 to produce FSD on the meter should be within the limits 4.8-5.2 volts. If it is not, adjust the value of meter series resistance until it is. Note that many anticlockwise turns of the trim pots may be necessary to reduce this test voltage to 5 V.

Add a really good 50 ohm dummy load to the output (type N 50 ohms 0.5 W and good to 1 GHz). Adjust both TP5 and TP6 to 2.06 volts using P5 and P6.

Switch off and add the pre-programmed PICAXE 28X2.

Switch on.

At start up, after the contrast trim pot is further adjusted to give the best display, the LCD should indicate the battery voltage within 5%. A few seconds later, it will indicate the frequency, load resistance (50 ohms), magnitude of load reactance (zero ohms) and SWR (1.00). Now switch through all the frequency ranges and check that the SWR remains under 1.05 and the indicated resistance stays within the range 48-52 ohms.

The reactance X should remain at zero. If all is well, go back to the lowest frequency range and load the output with a 0.25 W 150 ohm metal film resistor. A resistance of 150 ohms +/- 10% should be indicated with X=0. Also check using a 10 ohm resistor. Please note that the exact test point voltages required to produce the above results depend to a small degree on how well the resistance of the dummy load matches that of the internal 50 ohm current sensing resistor (R36//R37) and the relative matching of the diodes in the three envelope detectors.

Bluntly, you may have to play around very slightly with P5 and P6 to get the best compromise over the total frequency range. Note that the setup procedure forces the microprocessor to calculate and display a load resistance of 50 ohms, cancelling all tolerances in both the internal 50 ohms and dummy load, and so the analogue meter and LCD figures may not exactly agree. Tweaking P3 slightly can resolve this difference.

Both the indicated frequency and battery voltage may be slightly in error due to component tolerances.

See my website for the software tweaks to fix this.

Final comments

Having just waded through what is quite a complex set up process,

builders will probably be wondering why at VHF, when there is nothing attached to the N connector, the analyser does not show infinite SWR and an open circuit.

The answer is quite simple. Ordinary 50 ohm transmission line has a capacitance of around 100 pF/metre and an inductance of around 0.25 uH/metre, and the analyser has a permanently connected length of 50 ohm line (30-35 mm long) connected to its measurement bridge in the form of the N connector. So with nothing connected to the analyser the measurement bridge sees around 3-4 pF of connector and stray capacitance (250 ohms @ 160 MHz), while if you "short" the output, the analyser bridge sees around 8-9 nH of connector inductance (9 ohms @160 MHz). There are some small losses too which will also be indicated.

None of this really matters in normal measurements, because you used a nice 50 ohm N connector, instead of a horrible, anything but 50 ohm, SO239.

The 30-35 mm of connector length simply becomes part of the connecting transmission line and disappears. The connector length only becomes important in odd applications such as the making of phasing lines to connect multi antenna arrays together at VHF. In this case, you will have to make the phasing line 30-35 mm longer than

the analyser indicates.

Anyway, many congratulations.

You now have a piece of test gear which will conclusively demonstrate why the transistors in your transceiver final stage recently went pfffffft.

And really finally

My profound thanks to my two very good friends Barry Williams VK5BW and Wolf Langmair VK5WF, who waded through my initial drafts of material for this project, and somehow, despite the many errors I made, managed to construct two working prototypes, and tactfully tell me about my blunders at the same time. If you do make one of these analysers successfully, it is in no small way due to the efforts of these two.

References:

- VK5JST web site <http://www.users.on.net/~endsodds/> for printed circuit boards, software, photos and many more details.
- Adelaide Hills Amateur Radio Society website <http://www.ahars.com.au/> for a complete kit of parts.

Editor's Note: The Parts list and mechanical drawings can be found in the Digital Edition and on the WIA website:
<http://www.wia.org.au/members/armag/2015/december/>



Contribute



Articles and high quality photographs for *Amateur Radio* and *Callbook*.

See <http://www.wia.org.au/members/armag/contributing/>